

Assignment-1

Full mark-20

Q1. Consider the input voltage for the following circuit is a sine wave with a peak value of 10V.



- (a) Draw the V_{o1} and V_{o2} profiles from the circuit with proper label values.
- (b) Determine the difference between V_{o1} , V_{o2} and $(V_{o1}+V_{o2})$ voltage graphs.
- (c) Determine the average voltage value of V_{o1} .
- (d) Determine the peak inverse voltage of $D1$.

Q2. Design the clipper and clamper circuit to produce the following output voltage (V_o) according to the input voltage (V_i). Assume the diodes to be ideal.

